MOSFET as an Amplifer Printing Time:Wednesday, April 18, 2018, 9:01:07 PM -780m -740m -660m -700m -620m -580m -540m 600.0m 3.0 2.0 400.0m 200.0m - 1.0 Voltage across Drain Resistor Source Signal 0.0m -200.0m -400.0m -2.0 -600.0m -3.0 6.0m 7.0m 7.5m 8.0m 8.5m 5.0m 5.5m 6.5m 9.0m 4.5m Time (s)